



LAB REPORT

Khulna University of Engineering & Technology

Computer Science and Engineering

Name : Doniel Tripura

Roll : 1907121

Section : B

Semester : 2nd

Experiment No : 09



9 (1)
Experiment name: Study of Asynchronous Counter

AIM:

- (i) To design a 0 to 12 bit up counter.
- (ii) To design a 15 to 3 bit down counter.

Learning Objective:

- (i) To Learn about asynchronous counter and its application.
- (ii) To Learn the design of asynchronous up counter and down counter.

Components required:

IC 7476, Patch Cards & IC trainer kit

Theory:

A counter in which each flip flop is triggered by the output goes to previous flip-flop. As all the flip flops don't state change state simultaneously, spike occur at the output. To avoid this, strobe pulse is required. Because of propagation delay the operating

speed of asynchronous counter is low.

Asynchronous counters are easy and simple to construct.

Procedure:

- (i) All the components for their workings were checked.
- (ii) The appropriate IC into the IC base was inserted.
- (iii) Connections were made as shown in the circuit diagram.
- (iv) The truth table was verified and the outputs were also verified.

Truth Table for 0-12 up counter:

Counter state	Q_3	Q_2	Q_1	Q_0	Counter state	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0	7	0	1	1	1
1	0	0	0	1	8	1	0	0	0
2	0	0	1	0	9	1	0	0	1
3	0	0	1	1	10	1	0	1	0
4	0	1	0	0	11	1	0	1	1
5	0	1	0	1	12	1	1	0	0
6	0	1	1	0	13	0	0	0	0

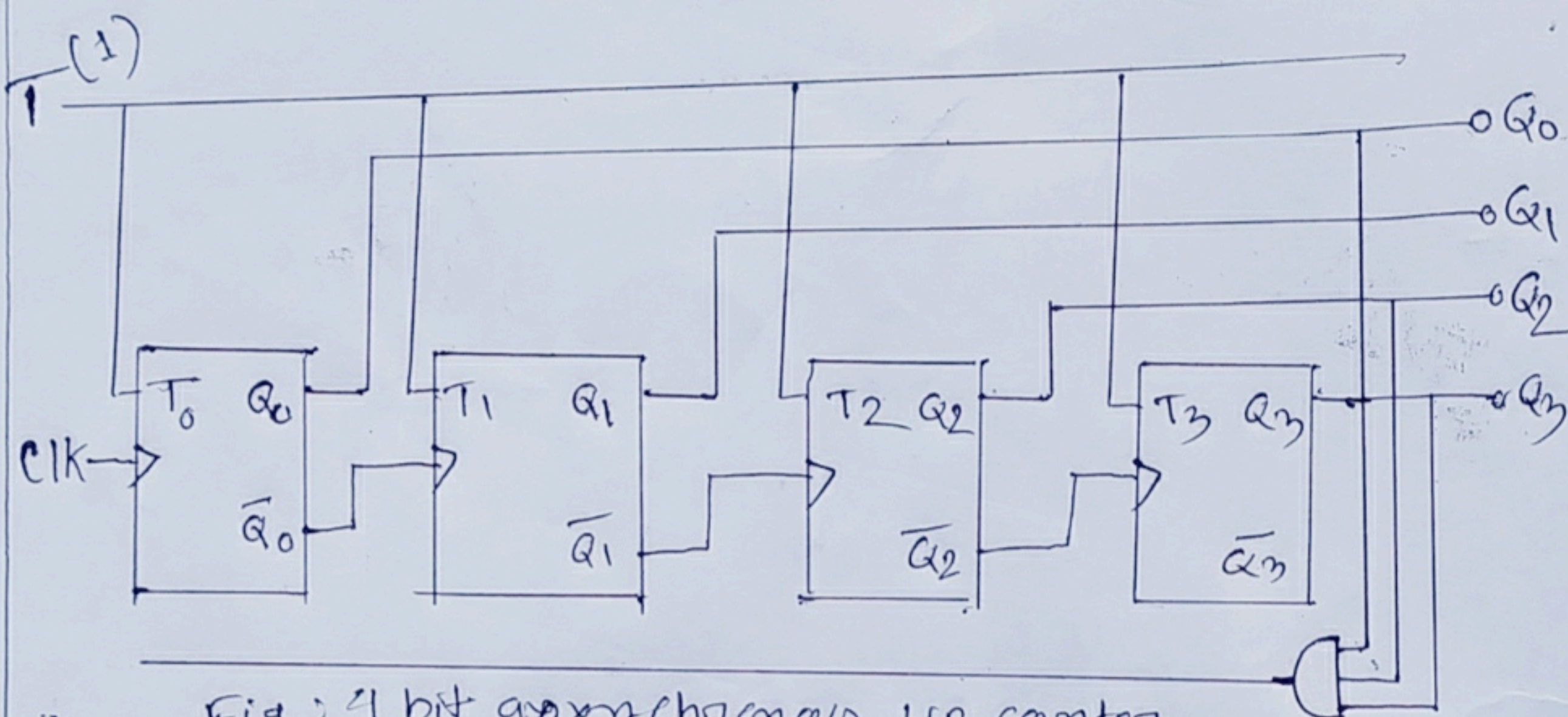


Fig : 4 bit asynchronous up counter

Truth Table for 4 to 3 down counter

Counter state	Q_3	Q_2	Q_1	Q_0	Counter state	Q_3	Q_2	Q_1	Q_0
15	1	1	1	1	8	1	0	0	0
14	1	1	1	0	7	0	1	1	1
13	1	1	0	1	6	0	1	1	0
12	1	1	0	0	5	0	1	0	1
11	1	0	1	1	4	0	1	0	0
10	1	0	1	0	3	0	0	1	1
9	1	0	0	1	2	0	0	1	1

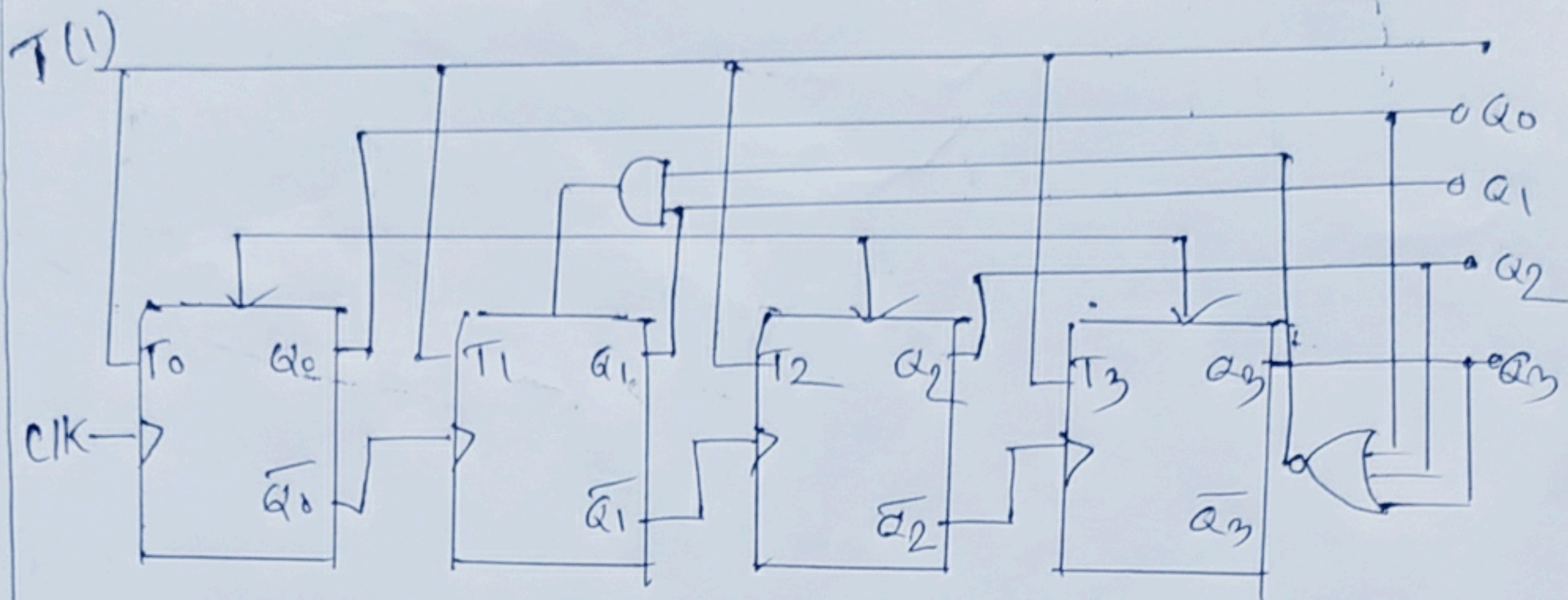


Fig : 4 Bit asynchronous Down Counter

Result : The working method of asynchronous counters is verified.

Viva question :

Q. What is an asynchronous counter?

Ans: The output of which sequential circuit counter is free from clock signal is called asynchronous counter.

Q. How is it different from synchronous counter?

Ans: In synchronous counter every flip-flops are connected with same clock signal, where in asynchronous counter flip flop are not connected to same clock signal, they separate their signal from previous output.