

Khulna University of Engineering and Technology

Computer Science and Engineering

Name : Doniel Tripura

Roll : 1907121

Section : B

Semester : 2nd Semester

Experiment No : 02

Experiment no:02

Enperiment name: Realization of a Doolean Function.

AIM: To simplify the given enplession and to stealize it using basic gates and universal gates.

Components staguired:

10 7400, 10 7408, 10.7406, 107402, Partch ands, FC. Triainer Kit.

Theory:
cononical sorms: Amy boolean sunction can be written in disjunctive or conjunctive normal form.

A boolean function can be represented by K-Haps in which each cell corresponds to a minterm. The cells are avvianged in such a way that any two immediately adjucent cells in such a way that any two corresponds to two minterms of distance.

a function of two variables, say f(x, y). Y' | f(0,0) | d(1,0) Y (f(0,1)) f(1) For a function of three variables, f (n, 4,2) n, h, nit sie nie, 21 f(0,0,0)f(0,1,0)f(0,10) f(1,00) Z [f(0,0,0)f(0,1),3(1,1)) 8(10,1), a function of four variables of (WXXX) win' win un wn' 4,5, 2(0'0'0') (0'0'0') (6'0'0') (6'0') (6'0') (9'0') 1/2 [5(0,1,0,0)) (a,10,1) for 1/1) for 1/1) 3 8(1,1,0,0) f(21,0,0) 8(1,1,1) 8(1,1,0) 0

Block diagrams of the 16s:

10 (7400) NAND Grate:

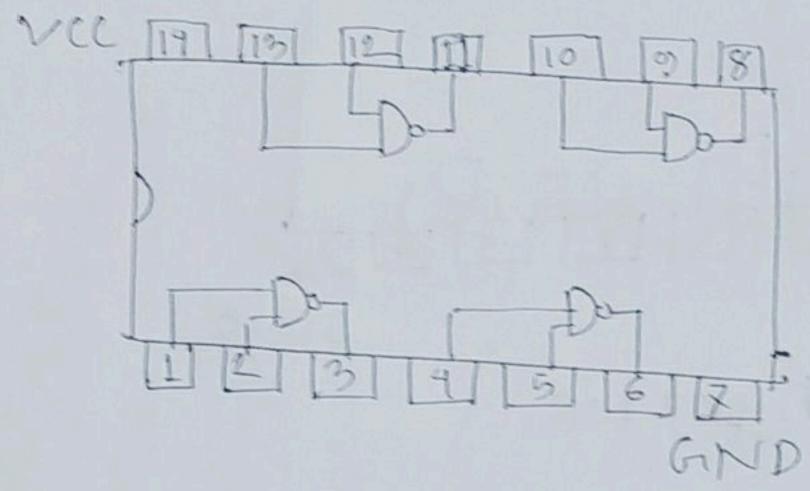


Fig. 10 7900

10 7402 (NOR Grate)

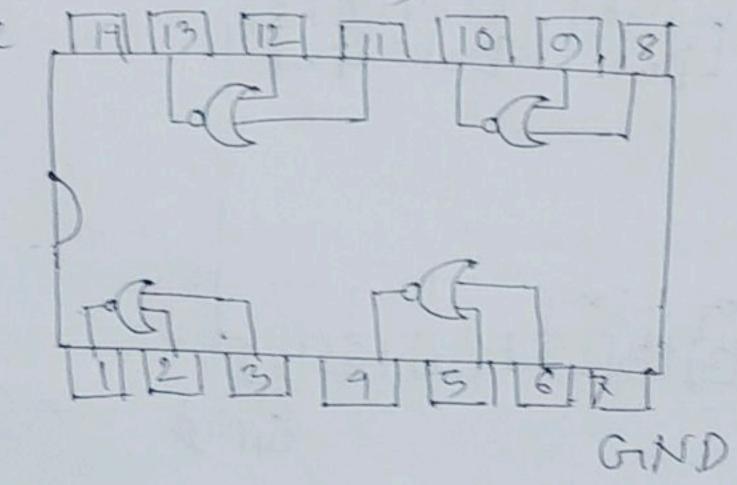


Fig: 107402

1C Z408 (AND Gate) 1 Fig:11(7,408 1C 7906 (NOT Grate) GND Fig:107406

10. (7432) ÖR Gale;

VCC MIDIPINION OF SILLING GND

FIG. 16. 7000

Fig:107432

Realization of Bookean Enpression:

Given, F=A'B'C'D'+A'B'CD+A'BCD+A'BCD +ABD+AB'C'D'+AB'CD'


= A'B'C'D'+ A'B'C D+A'BC'D+A'BCD+ABD(C+T)+AB'C'D' + AB'CD'

= A'B'C'D'+A'B'CD+A'BC'D+A'BC'D+ABC'D + AB'C'D'+AB'CD' Using, K-Map: method, the simplified expression.
F=BD+B'C'D'+A'CD+AB'D'

Truth Table of enpression:

Imput				Output ! Imput			Cutput		
A	B	C	D	F	A	B	C	D	F
0	0	0	0	1 - 1	1.	0	0	0	- 1
0	0	0	1)	0	1	0	0	1	0
0	0	1	0	0		0	1	0	4
0	0	111	10	o colora	18	0	1	1	0
0	d	0	0	0,0	1	1	0	o°	0'
. 0	1	0	(, ,	1	1	1-1	O	1	AFF DA
-0	1	i	0	0	1	P	11	0	0
0	t	1	1	1	1	1	1	(1

Realizing vying basic gates;

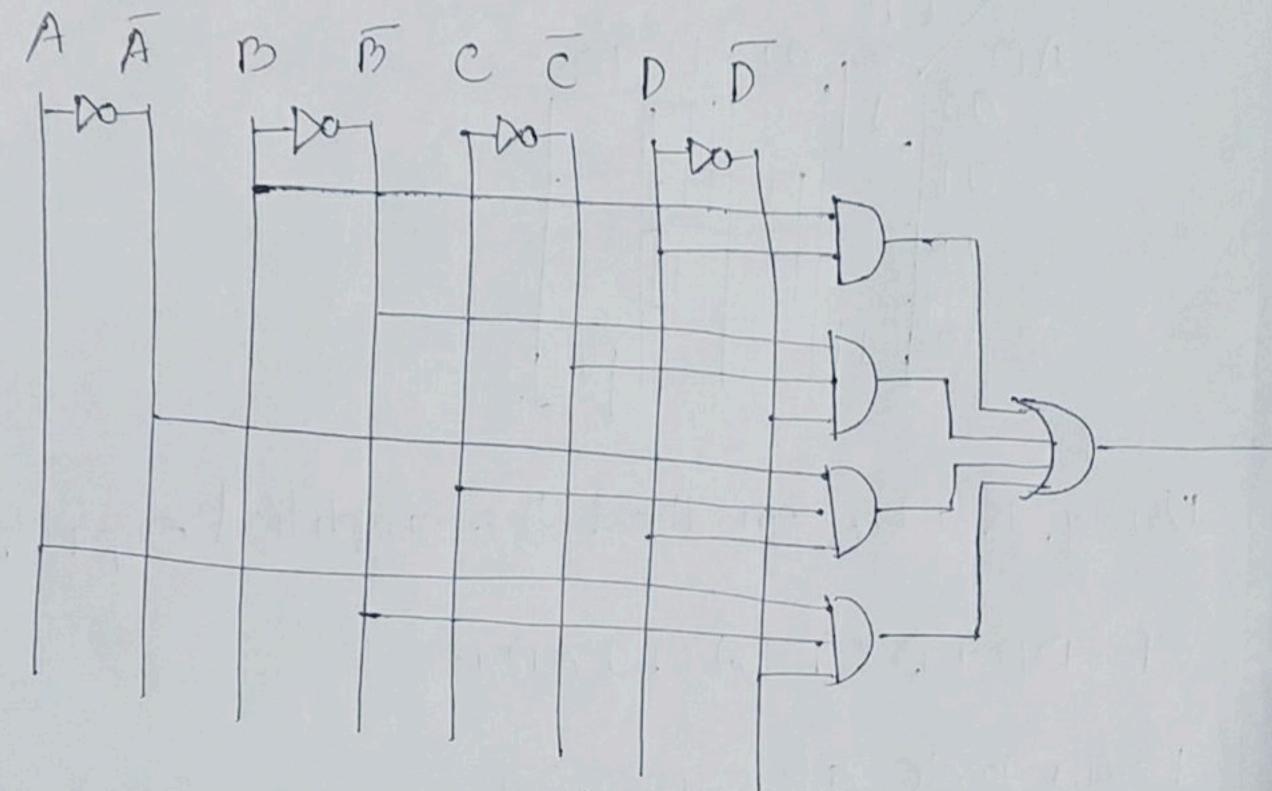

10 7406 used: 4 10 7408 used: 1 10 7432 used: 1


Here, F = BD + B'C'D' + A'CD + AB'D' = (BD + B'C'D' + A'CD + AB'D')'' $= (BD)' + (B'C'D')' \cdot (A'CD)' \cdot (AB'D')'$ $= (B'+D') \cdot (B'+C+D) \cdot (A+C'+D') \cdot (A'+B+D)'$ = (B'+D')' + (B+C+D)' + (A+C'+D')' + (A'+B+D)'

Realizing voing NAND Grate:

Total NAND Grate wed: 9)
Total 10 chips wed: 83

Here, = {(BD)'. (B'C'D')'. (A'CD). (AB'D')')'

Realise uning Nor Grate:

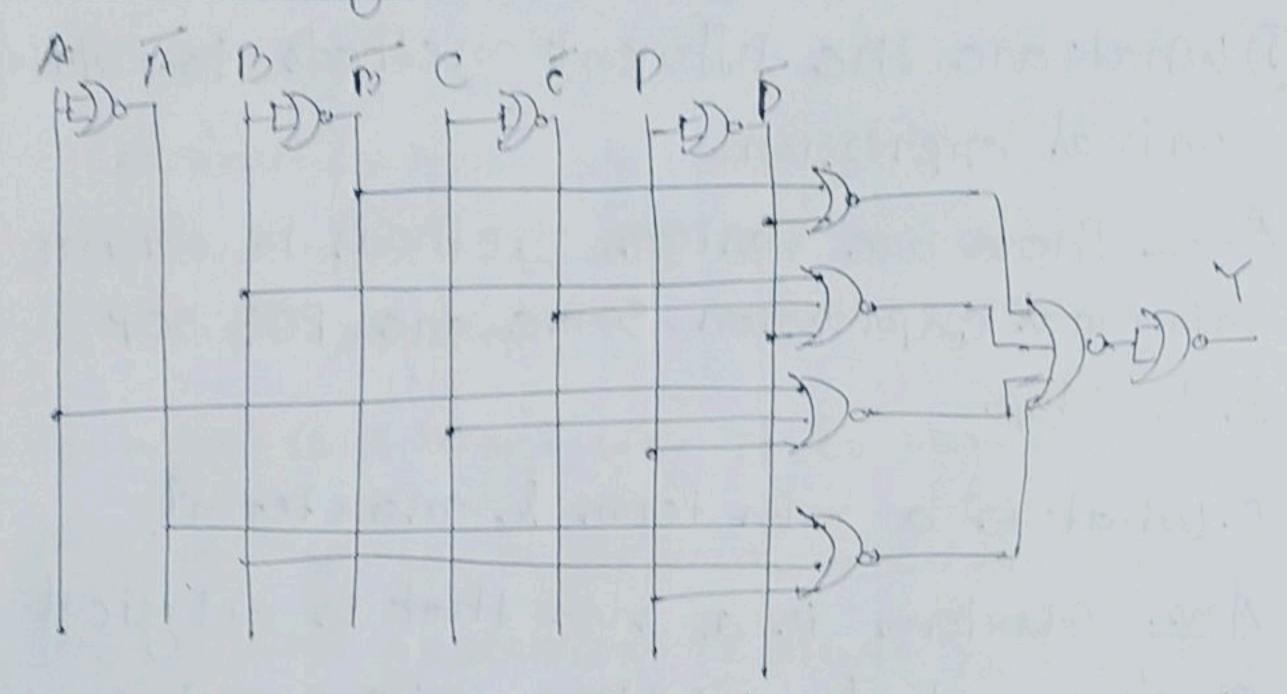

Total NOR Grat used: 10 Total IC Chips used: 3

Hene.
Y= { (B'+ D') + (B+ C+D)'+ (A+ C+D')+ (A+O+D)}"

Englished As with the Control of the

Viva question:

Dunat are the different methods its obtain minal expression.

Ans: There are various methods to obtain minimal enprezsion, some are, pos, sop & K-Map.

2. What is a min term & mon term?

Ansi 'Manterm' is a sum that is a logical or of a set of variables while mintermiss a product term in which each variables appears once.

9. State the difference between SUP & POS.

Ans: SOP is method of describing a booken enpression using a set of minterns or product terms. POS is a method of describing a boolean enpression using a set of man terms or sum terms.

4. What is meant by cononical representation?

Ansight is one which provides the simplest representation of an boolean in a unique way and which allows it to be identified in a mique way.

5. What is K-Map? why it is used?

Ans: K-Map is a pictorial method used to minimized expressions without howing to use boolean algebra theorems and equations gt is mostly used to simplify a boolean function.

6. What are the miversal gates?

Ansi NAND and NOR Grates are the iniversal gates.