



LAB REPORT

Khulna University of Engineering & Technology

Computer Science and Engineering

Name : Doniel Tripura

Roll : 1907121

Section : B

Semester : 2nd

Experiment No : 10



Experiment name: Decoders

AIM:

- (i) To realize a decoder circuit using basic gates.
- (ii) To design a full adder using decoder.

Learning Objectives:

- (i) To Learn about working principle of decoder.
- (ii) To Learn about the application of decoder.
- (iii) To Learn implementing 3 to 8 decoder.

Theory:

A decoder is a combinational circuit that connects the binary information from 'n' input lines to a maximum of 2^n unique output lines. Decoder is also called a minterm generator/maxterm generator. A minterm generator is constructed using AND and NOT gates. The appropriate output is indicated by logic (1) \rightarrow (positive logic \rightarrow T). Maxterm is constructed using logic 1 (positive logic).

Minterm is constructed using NAND gates.
The appropriate output is indicated by logic 0
(negative logic).

Truth Table for full Adder:

A	B	Cin	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	S	Car
0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	1	0	0	0	0	0	1	0
0	1	1	0	0	0	1	0	0	0	0	0	1
1	0	0	0	0	0	0	1	0	0	0	1	0
1	0	1	0	0	0	0	0	1	0	0	0	1
1	1	0	0	0	0	0	0	0	1	0	0	1
1	1	1	0	0	0	0	0	0	0	1	1	1


Here, $S = D_1 + D_2 + D_4 + D_7$

& $Car = D_3 + D_5 + D_6 + D_7$

Components required:

IC 7404, IC 7408, IC 7432, Patch cord &

Trainer kit

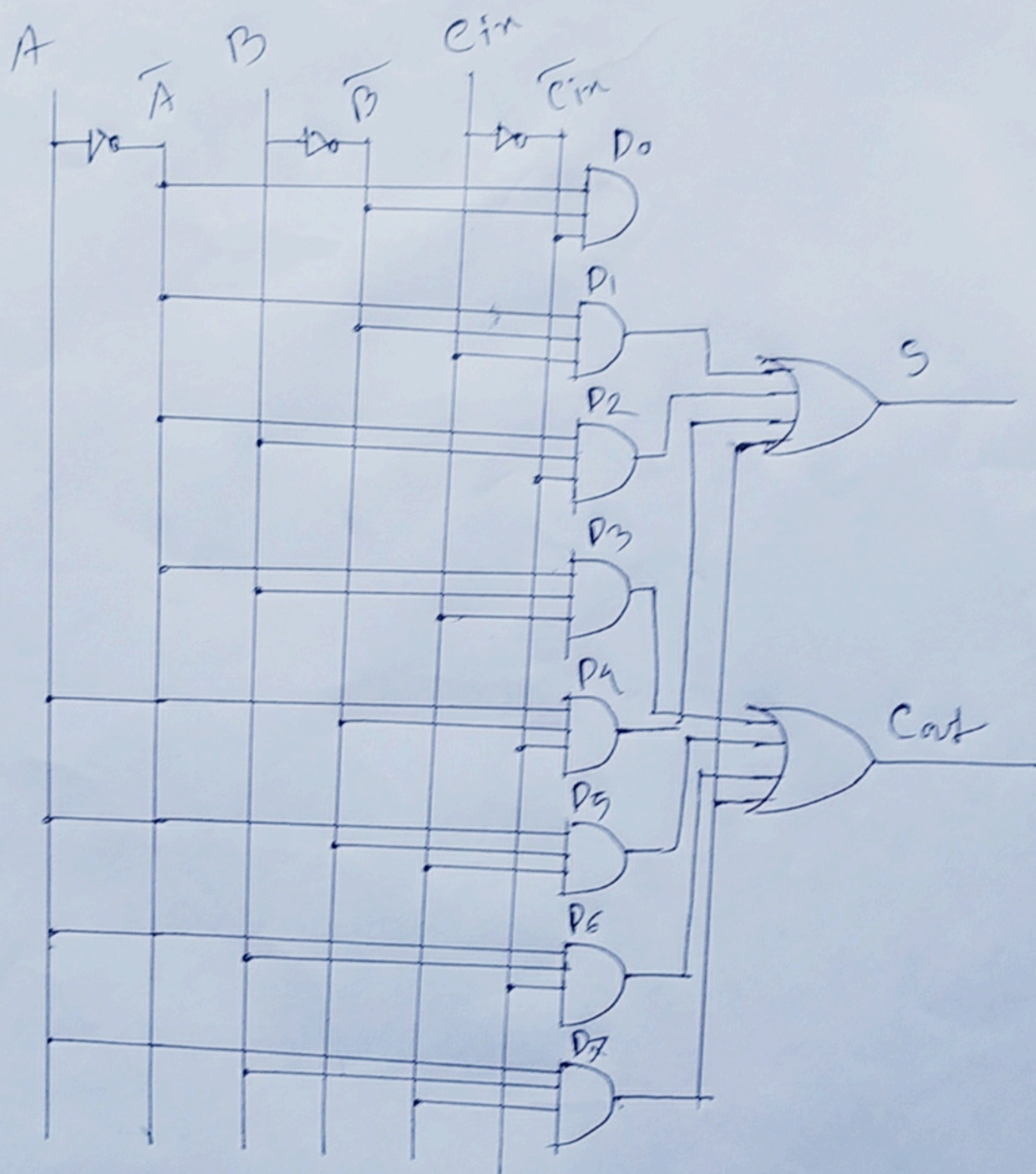

Procedure:

- (i) The connections were made as per the output circuit diagram.
- (ii) The values of A, B and C-in were changed using switches.

(iii) The output results were observed and the truth table was verified.

(iv) The whole procedure is maintained.

Result:

The operation of 3 to 8 decoder was verified.

Viva question:

Q. What are the applications of decoder?

Ans)

(i) These are used in analog to digital conversion is analog decoders.

(ii) To convert instructions into CPU we use decoder.

(iii) Mainly these are used in logical circuits and for data transferring.

Q. What is the difference between decoder and encoder?

Ans) Encoders convert digital data into binary data. On the other hand, decoders convert binary data into digital data.

Q. For $n \rightarrow 2^n$ decoder, how I/P lines & how many o/p lines are there?

Ans: input line $\rightarrow n$ output line $\rightarrow 2^n$

Q) What is the difference between decoder and demux?

Ans: A demux is a circuit that takes the input to several outputs depending on selection line. A decoder is a circuit that converts input signals or decodes the signals.